
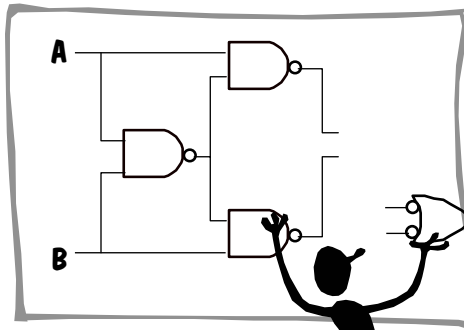


Gates and Combinational Logic

 

- 1) Combinational Timing Analysis
- 2) Lenient Gate Specifications
- 3) Universal Gates
- 4) Large Fan-in Gates
- 5) Logic Design Methodologies
- 6) Minimal SOP Realizations
- 7) Glitches & Static Hazards
- 8) Multiplexer Logic




Then we go home!



A Quick Review


- A **combinational device** is a circuit element that has
 - one or more digital inputs
 - one or more digital outputs
 - a **functional specification** that details the value of each output for every possible combination of valid input values
 - a **timing specification** consisting (at minimum) of an upper bound t_{PD} on the required time for the device to compute the specified output values from an arbitrary set of stable, valid input values

Static discipline

 


Delays, They're a Fact of Life

 Propagation delay (t_{PD}):
 An UPPER BOUND on the delay from valid inputs
 to valid outputs.




 A common design goal is to minimize propagation delay!



Contamination Delay

 INVALID inputs take time to propagate, too...




Do we really need t_{CD} ?

Usually not... it'll be important when we design circuits with registers (coming soon!). Sometimes you will see it spec'ed with the dubious name "minimum propagation delay".

If t_{CD} is not specified, safe to assume it's 0.


CONTAMINATION DELAY, t_{CD}
 A LOWER BOUND on the delay from any invalid input to an invalid output

The Combinational Contract

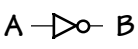

A	B
0	1
1	0

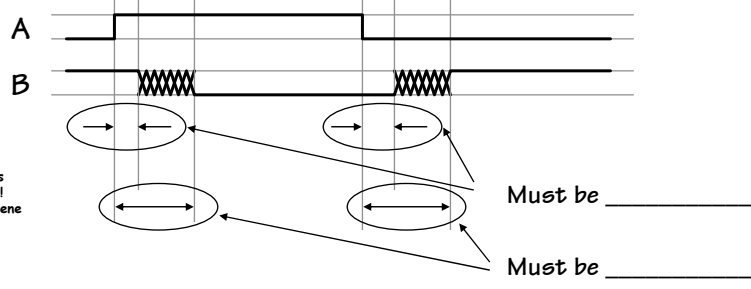t_{PD} propagation delay
 t_{CD} contamination delay



Must be _____
Must be _____

N.B:

1. No Promises during contamination
2. Default (conservative) spec: $t_{CD} = 0$

Comp 120 - Spring 2005
1/25/05
L04 - Combinational Logic 5


Example: Timing Analysis

If NAND gates have a $t_{PD} = 4nS$ and $t_{CD} = 1nS$

t_{CD} is the **minimum** cumulative contamination delay over all paths from inputs to outputs

$t_{PD} = \underline{\hspace{2cm}}$ nS


$t_{CD} = \underline{\hspace{2cm}}$ nS

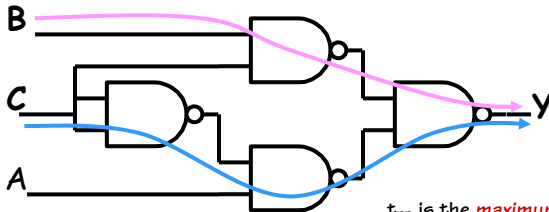

t_{PD} is the **maximum** cumulative propagation delay over all paths from inputs to outputs

Comp 120 - Spring 2005
1/25/05
L04 - Combinational Logic 6

One Last Issue...

 


Recall the rules for *combinational devices*:

Output guaranteed to be valid when **all** inputs have been valid for at least t_{pd} , and, outputs may become invalid no earlier than t_{cd} after an input changes!

Many gate implementations--e.g., CMOS—adhere to even tighter restrictions.

What Happens In This Case?

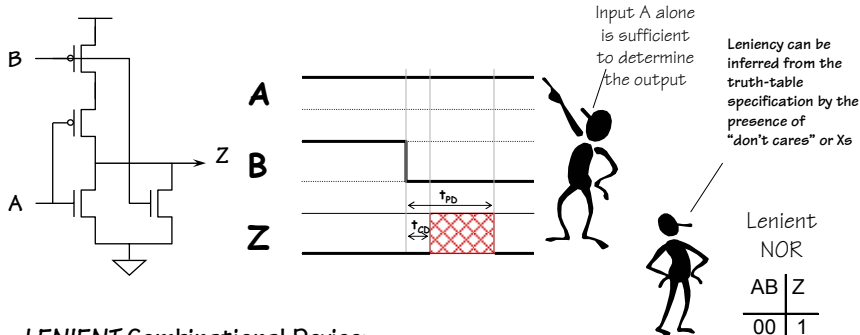


Leniency can be inferred from the truth-table specification by the presence of "don't cares" or Xs

Lenient NOR


AB	Z
00	1
X1	0
1X	0

 LENIENT Combinational Device:
Output guaranteed to be valid when any combination of inputs sufficient to determine output value has been valid for at least t_{pd} . Tolerates transitions -- and invalid levels -- on irrelevant inputs!



Now We're Ready to Design Stuff!

 We need to start somewhere -- usually it's the functional specification



Truth Table


C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

If you are like most scientist you'd rather see a formula than parse a logic puzzle. The fact is, **any combinational function can be expressed as a table.**

These "truth tables" are a concise description of the combinational system's function. Conversely, **any computation performed by a combinational system can be expressed as a truth table.**

Where Do We Start?

We have a bag of gates.

 

We have a spec.

What do we do?

Did I mention we have gates?

We need

... a systematic approach for designing logic

A Slight Diversion

Are we sure we have all the gates we need?
 Just how many two-input gates are there?

AND		OR		NAND		NOR	
AB	Y	AB	Y	AB	Y	AB	Y
00	0	00	0	00	1	00	1
01	0	01	1	01	1	01	0
10	0	10	1	10	1	10	0
11	1	11	1	11	0	11	0



Hum... all of these have 2-inputs (no surprise)
 ... each with 4 permutations, giving 2² output cases
 How many permutations of 4 outputs are there? ____

There Are Only So Many Gates

There are only 16 possible 2-input gates
 ... some we know already, others are just silly




I N P	Z	X	N	N	N	N	N									
U	E	A	A	B	X	N	O	A	O	B	A	O				
T	R	N	>	>	O	O	O	O	T	<=	T	<=	N	N		
AB	O	D	B	A	A	B	R	R	R	R	'B'	'B'	'A'	A	D	E
00	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
01	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
10	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
11	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

Do we need all of these gates?
Nope. After all, we describe them all using AND, OR, and NOT.

We Can Make Most Gates Out of Others

B > A		Y
AB		
00		0
01		1
10		0
11		0


XOR		Y
AB		
00		0
01		1
10		1
11		0

   

How many different gates do we really need?

One Will Do!


NANDs and NORs are universal

 

Ah!, but what if we want more than 2-inputs

Stupid Gate Tricks

Suppose we have some 2-input XOR gates:

 


$$t_{pd} = 1$$

$$t_{cd} = 0$$

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

And we want an N-input XOR:

 


output = 1
iff number of 1s
input is ODD
("ODD PARITY")

$$t_{pd} = O(\text{---}) \text{ -- WORST CASE.}$$

Can we compute N-input XOR faster?

 I Think That I Shall Never See a Gate Lovely as a ...



N-input TREE has $O(\text{---})$ levels...


Signal propagation takes $O(\text{---})$ gate delays.

Question: Can EVERY N-Input Boolean function be implemented as a tree of 2-input gates?


Are Trees Always Best?

Alternate Plan: Large Fan-in gates

 - ◆ N pulldowns with complementary pullups
- ◆ Output HIGH if any input is HIGH = “OR”



 - ◆ Propagation delay: $O(\text{_____})$
since each additional MOSFET adds C



Don't be misled by the “big O” stuff... the constants in this case can be much smaller... so for small N this plan might be the best.

Here's a Design Approach

Truth Table

C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

- 1) Write out our functional spec as a truth table
- 2) Write down a Boolean expression for every ‘1’ in the output

$$Y = \overline{C}BA + \overline{C}B\overline{A} + C\overline{B}\overline{A} + CBA$$

- 3) Wire up the gates, call it a day, and go home!

This approach will always give us logic expressions in a particular form: SUM-OF-PRODUCTS

- it's systematic!
- it works!
- it's easy!
- we get to go home!




Straightforward Synthesis

We can implement
 SUM-OF-PRODUCTS
 with just three levels of
 logic.

INVERTERS/AND/OR

 Propagation delay --
 No more than 3 gate delays
 (ignoring fan-in)



Logic Simplification

Can we implement the same function with fewer gates?

Before trying we'll add a few more tricks in our bag.

RULES BOOLEAN ALGEBRA:

OR rules: $a + 1 = 1, a + 0 = a, a + a = a$

AND rules: $a1 = a, a0 = 0, aa = a$

Commutative: $a + b = b + a, ab = ba$

Associative: $(a + b) + c = a + (b + c), (ab)c = a(bc)$

Distributive: $a(b+c) = ab + ac, a + bc = (a+b)(a+c)$

Complements: $a + \bar{a} = 1, a\bar{a} = 0$

Absorption: $a + ab = a, a + \bar{a}b = a + b$
 $a(a+b) = a, a(\bar{a}+b) = ab$

Reduction: $ab + \bar{a}b = b, (a+b)(\bar{a}+b) = b$

DeMorgan's Law: $\overline{a+b} = \bar{a}\bar{b}, \overline{\bar{a}\bar{b}} = a+b$

Minimal Sum-of-Products

Once a logic expression is in Sum-of-Product (SOP) form, it is easy to minimize it further. In fact, we can reduce it to minimal set of products.

Here's the trick:

Factor out common terms and collapse groups of "don't care" bits.

$$\begin{aligned} Y &= \overline{C}\overline{B}A + \overline{C}B\overline{A} + C\overline{B}\overline{A} + CBA \\ Y &= \overline{C}A(\overline{B} + B) + CB(\overline{A} + A) \\ Y &= \overline{C}A + CB \end{aligned}$$

How do we find these "don't care" groups




A Geometric Approach

It is easy to identify clusters of "don't care" bits geometrically.

Products with these clusters, have terms that differ in exactly one bit position. So if we could arrange all possible products so that those which differ by exactly one bit are adjacent to one another then we could see these clusters easily.

 We've seen such an arrangement of codings before when we computed Hamming distances.



Karnaugh Maps


Here's the layout of a 3-variable K-map filled in with the values from our truth table

C \ AB	B		A	
	00	01	11	10
0	0	0	1	1
1	1	0	1	0

It's cyclic. The left edge is adjacent to the right edge. (It's really just a flattened out cube).

Jump to Hyperspace

 4-variable K-map for a multipurpose logic gate:



$$Y = \begin{cases} A \cdot B & \text{if } CD = 00 \\ A + B & \text{if } CD = 01 \\ \bar{B} & \text{if } CD = 10 \\ A \oplus B & \text{if } CD = 11 \end{cases}$$

CD \ AB	AB			
	00	01	11	10
00	0	0	1	0
01	0	1	1	1
11	0	1	0	1
10	1	0	0	1

Again it's cyclic. The left edge is adjacent to the right edge, and the top is adjacent to the bottom.

Finding Subcubes

We can identify clusters of “don’t care” bits by circling adjacent subcubes of 1s. A subcube is just a lower dimensional cube.

C\AB	00	01	11	10
0	0	0	1	1
1	0	1	1	0

\AB CD\	00	01	11	10
00	0	0	1	0
01	0	1	1	1
11	0	1	0	1
10	1	0	0	1

The best strategy is generally a greedy one.

Find, the largest subcube and circle it first. Continue circling the largest subcubes possible (even if it has some overlap with a previous one). Then proceed onto smaller and smaller subcubes until no 1s are left.

Write Down Equations

Write down a product term for the portion of each cluster/subcube that is invariant.

C\AB	00	01	11	10
0	0	0	1	1
1	0	1	1	0

$$Y = \bar{C}A + CB$$

This must be all
Let's go home!



\AB CD\	00	01	11	10
00	0	0	1	0
01	0	1	1	1
11	0	1	0	1
10	1	0	0	1

$$Y = ABC\bar{C} + \bar{A}BD + A\bar{B}D + \bar{B}C\bar{D}$$

Review: K-map minimization

- 1) Copy truth table into K-Map
- 2) Identify subcubes,
 - selecting the largest available at each step (even if it involves some overlap) until all ones are covered
- 3) Write down the answer


Does it always work? Not really...
There's still a bit of art to it

The circled terms are called *implicants*. An implicant not completely contained in another implicant is called a *prime implicant*.

C\AB	00	01	11	10
0	0	0	1	1
1	0	1	1	0

Are K-maps Really All That Useful?


- ◆ They are only manageable for small circuits (4-5 inputs at most)
- ◆ Sometimes you pick the wrong set of subcubes
- ◆ There are better techniques (better for computer's that is)
- ◆ SOP realizations aren't all that relevant
- ◆ We've got gates to burn
- ◆ Low fan-in gates are better suited to current technologies that SOP (FPGAs, Standard Cells)
- ◆ Sometimes minimal circuits are glitchy (more about this later)
- ◆ Some important circuits aren't amenable to minimal SOP realizations

 

That Gate has a Name!



The gate we've been designing for this entire lecture is a relatively important one.

Truth Table

 



C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

2-input Multiplexer

  

A Case for Non-Minimal SOP


$$Y = \bar{C}A + CB$$

  

C\BA	00	01	11	10
0	0	1	1	0
1	0	0	1	1

NOTE: The steady state behavior of these circuits is identical. They differ in their transient behavior.

$$Y = \bar{C}A + CB + AB$$

 

Lenient Mux

C	B	A	Y
0	X	0	0
0	X	1	1
1	0	X	0
1	1	X	1
X	0	0	0
X	1	1	0

If you include equations for all prime implicants, the resulting implementation will be lenient. Now can we go home?



Useful Gate Structures

NAND-NAND

$\overline{AB} = \overline{A+B}$

"Pushing Bubbles"

$\overline{xyz} = \overline{x + y + z}$

NOR-NOR

$\overline{AB} = \overline{A+B}$

$x + y = \overline{\overline{xy}}$

Comp 120 - Spring 2005
1/25/05
L04 - Combinational Logic 31

More Useful Gate Structures

AOI (AND-OR-INVERT)

$\overline{AB + CD}$

OAI (OR-AND-INVERT)

$\overline{(A+B)(C+D)}$


An OAI's DeMorgan equivalent is usually easier to think about.

AOI and OAI structures can be realized using a single CMOS gate. However, their function is equivalent to 3 levels of logic.

Comp 120 - Spring 2005
1/25/05
L04 - Combinational Logic 32

Logic That Defies SOP Realization

C_i	A	B	S	C_o
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

S	C/AB	00	01	11	10
0	0	0	1	0	1
1	1	0	1	0	

C_o	C/AB	00	01	11	10
0	0	0	0	1	0
1	0	1	1	1	

$$S = \bar{A}\bar{B}C_i + \bar{A}B\bar{C}_i + A\bar{B}\bar{C}_i + ABC_i$$

$$C_o = A\bar{B}C_i + \bar{A}BC_i + \bar{A}B\bar{C}_i + ABC_i$$

Looks like parity to me




Can simplify the carry out easy enough, eg...

$$C_o = BC + AB + AC$$

But, the sum, S, doesn't have a simple sum-of-products implementation even though it can be implemented using only two 2-input gates.


Logic Synthesis Using MUXes

 


2-input Multiplexer

Truth Table

C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 


schematic

 

Gate symbol

A 4-input Mux implemented as a tree

 


Systematic Implementation of Combinational Logic

Consider implementation of some arbitrary Boolean function, $F(A,B)$

... using a MULTIPLEXER as the only circuit element:


A	B	C_{in}	C_{out}
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

Small Improvements

We can also apply certain optimizations to MUX Logic

A	B	C_{in}	C_{out}
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

- Largely by inspection or exhaustive search

- N-input gate with N-1 input MUX & one inverter



Summary

- Timing specs
 - t_{PD} : upper bound on time from valid inputs to valid outputs
 - t_{CD} : lower bound on time from invalid inputs to invalid outputs
 - If not specified, assume $t_{CD} = 0$
- Combinational logic
 - Any function that can be specified by a truth table
 - Expressed in terms of AND/OR/NOT
 - Minimally, we can get away with just 2-input NANDs or NORs
 - Max number of inputs = 4? Then use multiple levels of logic
- Sum-of-products canonical form
 - Comes directly from truth table
 - “3-level” implementation of any logic function
 - Limitations on number of inputs (fan-in) increases depth

Now we
go home!

